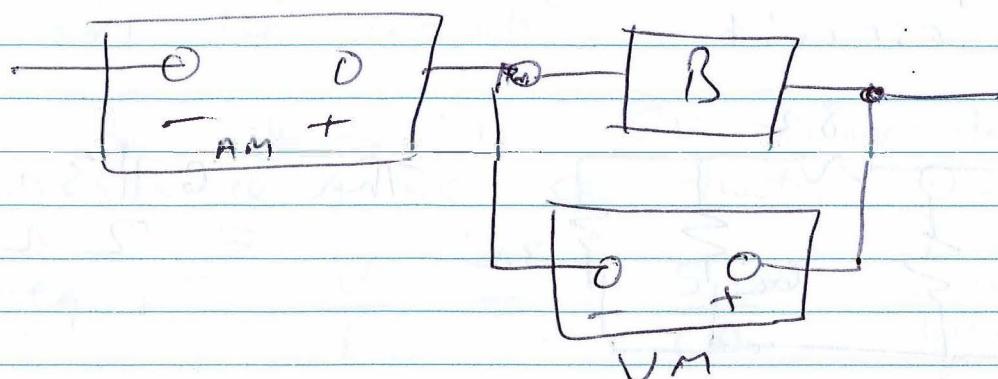


M1 D TEST SOLUTIONS

(1)



(a) Reference cannot enter the (+) node at the ammeter. This is also the (+) node of the Voltmeter.
Hence Passive Sign convention applies
MUST BE FULLY CORRECT [3]

(b) Since PSC applying, we have


$$\begin{aligned} P &= V I' \\ &= (-10V)(3A) \\ &= -30W \\ &< 0. \end{aligned}$$

Since Power is negative, device B generating energy.


MUST BE FULLY CORRECT

2


(2) (a) Reduce by adding a short circuit

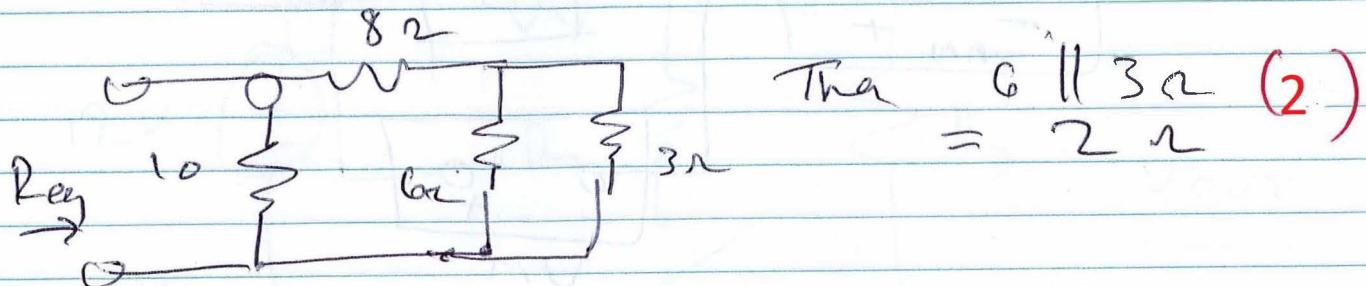

So we obtain

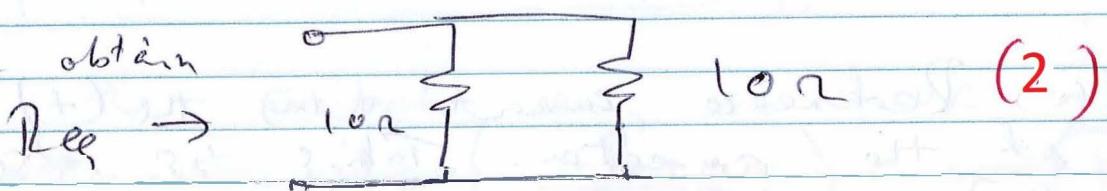

Thus $\text{Req} = 5 \Omega$.

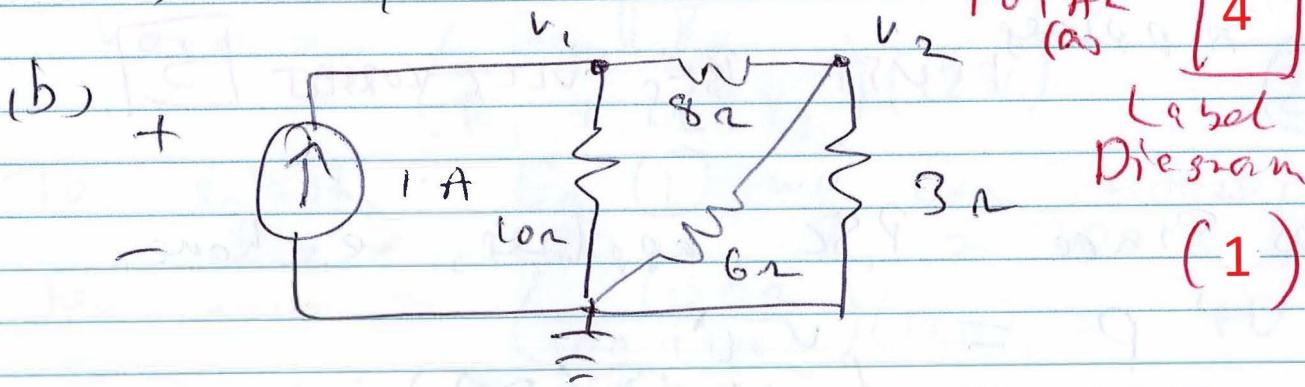

$$\text{ICCL node } 1 : 1A = \frac{v_1}{10\Omega} + \frac{v_1 - v_2}{8\Omega} \quad (1)$$

$$\text{ICCL node } 2 : 0 = \frac{v_2 - v_1}{8\Omega} + \frac{v_2}{6\Omega} + \frac{v_2}{3\Omega} \quad (2)$$

$$\text{Rewrite : } 1A = \frac{4v_1 + 5v_2 - 5v_1}{40} \quad (1)$$

$$\Rightarrow 40 = 9v_1 - 5v_2$$

$$\text{Rewrite } 0 = \frac{(3v_2 - 3v_1) + 4v_2 + 8v_2}{24} \quad (2)$$

$$\Rightarrow 0 = \frac{15v_2 - 3v_1}{40} - \frac{9v_1}{40} \quad (1)$$

$$\Rightarrow 40 = 45v_2 - 9v_1 \Rightarrow v_2 = 1 \quad (1)$$

$$\Rightarrow 9v_1 = 40 + 5 \Rightarrow v_1 = 5 \text{ V} \quad (1)$$

$$= 45 \quad (1) \text{ TOTAL } [7]$$

(2) So $v_1 = 5V$, is the voltage across the inputs.

(c) Since there is $5V$ across the $1A$ source, we see that most have ^{correct} V and I than (b)

$$R_{eq} = \frac{V}{I} = \frac{5V}{1A} = 5\Omega$$

(c) [1]

which confirms ^{our} answer to part (a).

TOTAL 4(2) [12]

(3) (a) Brown | Black | Black | Brown | Red
 $= 1 | 1 0 1 0 1 | 1 2$
 $= 100 \times 10^3 \pm 20\%$
 $= 1 k\Omega \pm 20\%$

MUST BE FULLY CORRECT

[2]

(b) $6.8mH = 6800 \mu H \pm 20\%$
 $= 68 \times 10^2 \mu H \pm 20\%$
 $= \text{Blue} | \text{Grey} | \text{Red} | \text{Red}$
MUST BE FULLY CORRECT


[2]

(c) $3.3mF = 3300 \text{ pF} \pm 5\%$
 $= 33 \times 10^2 \text{ pF} \pm 5\%$
 $= 332 \text{ F}$

[2]

MUST BE FULLY CORRECT.

TOTAL ③ [6]

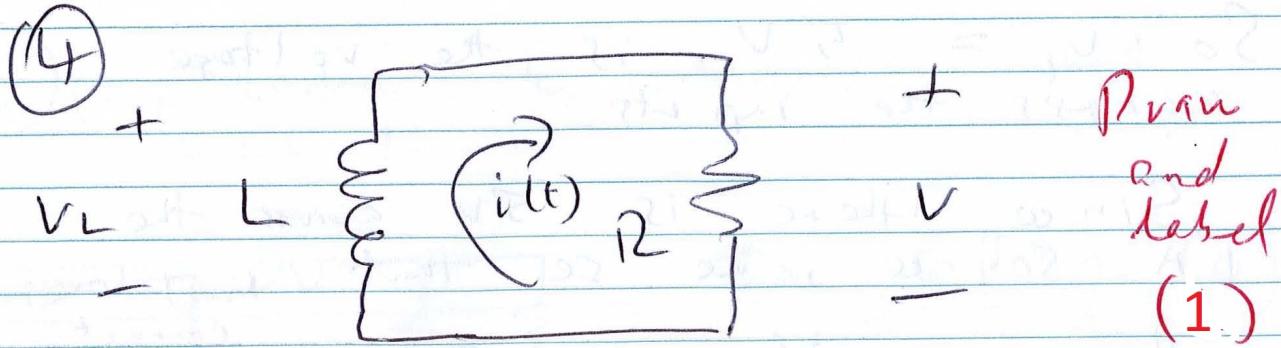

KVL : $V_L = V$ (1)

loop OHM'S LAW: $V = R i(0)$ (1)

Inductor Equation $V_L = -L \frac{di}{dt}$ (1)

or ASL applies to inductor. (1)

Obtain

$$0 = L \frac{di}{dt} + R i(t) \quad (1)$$

$i(0) = I_0.$

Solution is $i(t) = K_1 + K_2 e^{st}$ (1)

$$\frac{di}{dt} = s K_2 e^{st}$$

$$\begin{aligned} \text{So } 0 &= s L K_2 e^{st} + R K_1 + R K_2 e^{st} \\ &= R K_1 + K_2 (s L + R) e^{st} \end{aligned}$$

$$\Rightarrow 0 = K_1 \quad (1)$$

$$0 = s L + R$$

$$\Rightarrow s = -\frac{R}{L} \quad (1)$$


$$\Rightarrow i(t) = K_2 e^{-\frac{tR}{L}} \quad (1)$$

$$i(0) = K_2 = I_0 \quad (1)$$

$$\Rightarrow i(t) = I_0 e^{-\frac{Rt}{L}} \quad (1)$$

$$\Rightarrow V(t) = R i(t) = R I_0 e^{-\frac{Rt}{L}} \quad (1)$$

TOTAL (4): 13

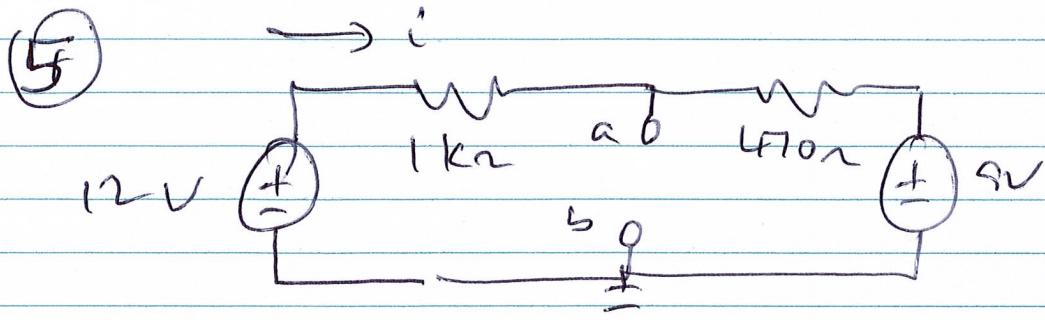

$$\begin{aligned}
 \text{(a) KVL} \quad 0 &= -12V + 1.47i + 9V \\
 \text{loop: } \Rightarrow 3V &= 1.47i \quad (\text{in mA}) \\
 \Rightarrow i &= 2.048 \text{ mA} \\
 \text{Hence } V_a &= 12V - (1k\Omega)(2.048 \text{ mA}) \\
 &= 9.96 \text{ V. (2)} \\
 &= V_{OC}
 \end{aligned}$$


To find IT , we can 'switch off' the independent voltage sources.'

$$1\text{ k}\Omega \quad \left. \begin{array}{c} | \\ \text{---} \\ | \end{array} \right\} 6 \quad \left. \begin{array}{c} | \\ \text{---} \\ | \end{array} \right\} 470 \quad R_T = 1\text{ k}\Omega \parallel 470\Omega$$

$$= 320\Omega \text{, (2)}$$

$$\Rightarrow I_{SL} = \frac{V_{OC}}{R} = 31.1 \text{ mA. (1)}$$

NORTON
CIRCUIT

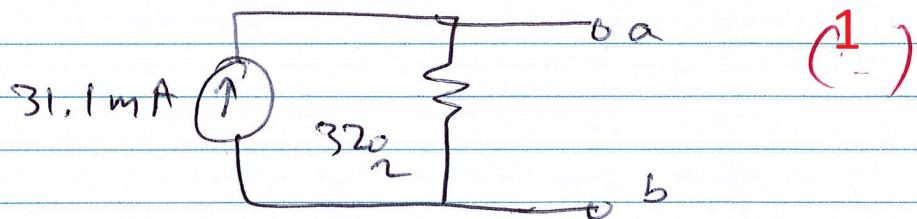

(b) Attach Load
Tension

TOTAL (a)

6

$$(b) \quad T_{\text{first to}} \rightarrow i_2 = 20 \text{ mA}$$



$$I_{RL} = \frac{20mA}{31.1mA} = \frac{320}{320+R_L} \quad (2)$$


$$\Rightarrow \underline{320 + R_L} = 497.6$$

$$\Rightarrow R_L = 177 \cdot 6 \Omega$$

yield 20 mA of current in the load resistor **Total(b)**

4

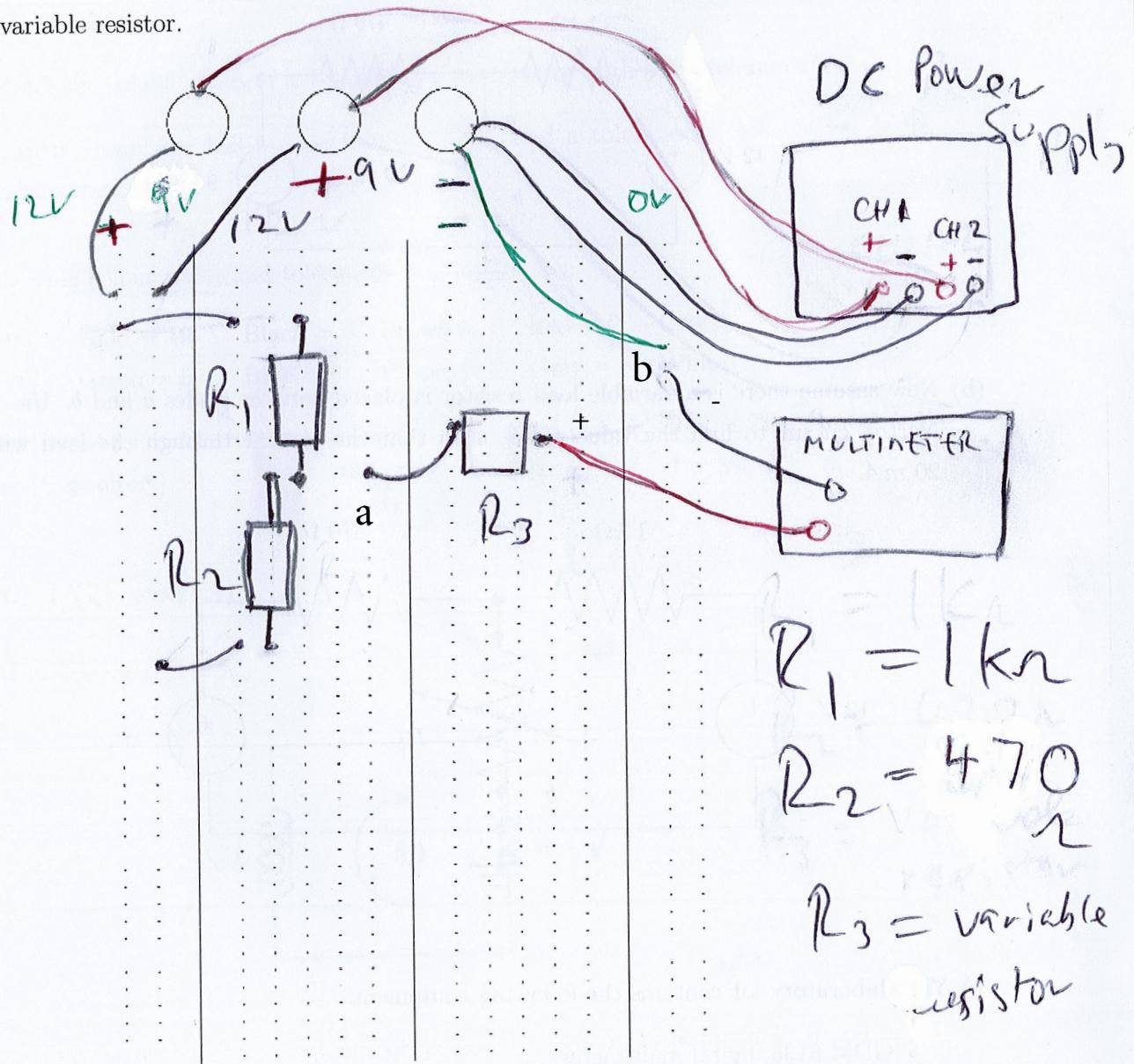Use the Breadboard diagram below to show how you would build and measure the circuit in Question (b) on your breadboard. Draw and label the input voltage terminals, the resistors (these may be drawn as rectangular boxes) and the connecting wires. Show where you would place the multimeter probes in order to measure the current through the variable resistor.



$$R_1 = 1\text{ k}\Omega$$

$$R_2 = 470\text{ }\Omega$$

R_3 = variable
resistor

TOTAL (c)

4

TOTAL (d)

14